

Summary


- Language introduction / flow
- Simple examples
- Advanced examples
- Meta-hardware description examples

Language introduction

- Open source, started in december 2014
- Focus on RTL description
- Thinked to be interoperable with existing tools
 - It generate VHDL/Verilog files
 - It can integrate VHDL/Verilog IP as blackbox
- Abstraction level :
 - You can design things similary to VHDL/Verilog
 - If you want to, you can use many abstraction utils and also define new ones

Language flow

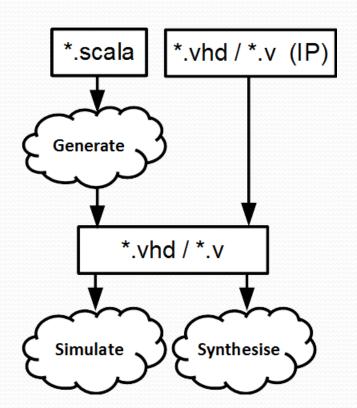
- 1. Describe your RTL
- 2. Generate the VHDL/Verilog
- 3. Simulate and synthesize



Some points about Spinal

- There is no logic overhead in the generated code. (I swear!)
- Spinal HDL is a RTL language. But the generated VHDL/Verilog is simulatable with all standards EDA tools.
- The component hierarchy and all names are preserved during the VHDL/Verilog generation.

Simple examples

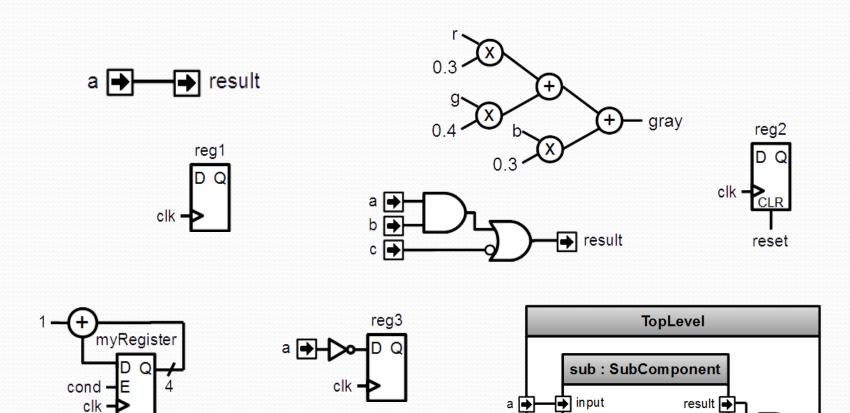

b **→**

result

A simple component

Combinatorial logic

```
class MyComponent extends Component {
  val io = new Bundle {
    val a = in Bool
    val b = in Bool
    val c = in Bool
    val result = out Bool
  }

io.result := (io.a & io.b) | (!io.c)
}
```

Signals

```
class MyComponent extends Component {
  val io = new Bundle {
    val a
              = in Bool
    val b
             = in Bool
    val c = in Bool
    val result = out Bool
  val a_and_b = Bool
  a_and_b := io.a & io.b
                                               a and b
                                                         → result
  val not_c = ! io.c
  io.result := a_and_b | not_c
```

Generated VHDL

```
class MyComponent extends Component {
  val io = new Bundle {
    val a = in Bool
    val b = in Bool
    val c = in Bool
    val result = out Bool
  }
  val a_and_b = io.a & io.b
  val not_c = !io.c
  io.result := a_and_b | not_c
}
```

```
entity MyComponent is
  port(
    io_a : in std_logic;
    io b: in std logic;
    io_c : in std_logic;
    io result : out std logic
  );
end MyComponent;
architecture arch of MyComponent is
  signal a_and_b : std_logic;
  signal not c: std logic;
begin
  io_result <= (a_and_b or not_c);</pre>
  a and b <= (io a and io b);
  not_c <= (not io_c);
end arch;
```

Registers

```
class MyComponent extends Component {
  val io = new Bundle {
    val a = in Bool
                                    reg1
  val reg1 = Reg(Bool)
                                                  reg2
  val reg2 = Reg(Bool) init (False)
  val reg3 = Reg(Bool)
                                                  reset
  reg3 := ! io.a
                                    reg3
```

No more Process/Always blocks

```
cond - mySignal
val mySignal
                           = Bool
                           = Reg(UInt(4 bits))
val myRegister
val myRegisterWithReset
                           = Reg(UInt(4 bits)) init(0)
                                                                     myRegister
                                                                  cond
mySignal := False
when(cond) {
  mySignal
                        := True
                                                                 myRegisterWithReset
  myRegister
                        := myRegister + 1
  myRegisterWithReset := myRegisterWithReset + 1
                                                                 cond -
                                                                       reset
```

Component internal organisation

```
class TopLevel extends Component {
    //...
    val logicArea = new Area {
        val flag = Bool
    }

    val fsmArea = new Area {
        when(logicArea.flag) {
            //...
        }
    }
}
```

Component instance

io.result := sub.io.result | io.b

```
class SubComponent extends Component{
  val io = new Bundle {
    val input = in Bool
    val result = out Bool
                                                                TopLevel
                                                      sub: SubComponent
class TopLevel extends Component {
  val io = new Bundle {
                                                    input input
                                                                      result 🗪
                                             a →
    val a
              = in Bool
                                                                                          result
    val b
          = in Bool
    val result = out Bool
  val sub = new SubComponent
  sub.io.input := io.a
```

UInt, Vec, When

```
class MyComponent extends Component
  val io = new Bundle {
    val conds = in Vec(Bool,2)
    val result = out UInt(4 bits)
  when(io.conds(0)){
    io.result := 2
    when(io.conds(1)){
      io.result := 1
  } otherwise {
    io.result := 0
```



Enum, Switch

```
object MyEnum extends SpinalEnum {
 val state0, state1 = newElement()
class MyComponent extends Component {
  val state = Reg(MyEnum) init(MyEnum.state0)
  switch(state) {
    is(MyEnum.state0) {
    is(MyEnum.state1) {
    default{
```

For, Variable, Generics

```
class CarryAdder(size: Int) extends Component {
  val io = new Bundle {
    val a
               = in UInt (size bits)
    val b = in UInt (size bits)
    val result = out UInt (size bits)
  var c = False
  for (i <- 0 until size) {</pre>
    val x = io.a(i)
    val y = io.b(i)
    io.result(i) := x ^ y ^ c
    c = (x \& y) | (x \& c) | (y \& c);
```

Latch/Loop

```
val a = Bool
val result = Bool
result := a | result //Loop detected

val result = Bool
when(cond){    //result is not assigned in all cases => Latch detected
    result := True
}
```

ClockDomains

```
class MyTopLevel extends Component {
  val io = new Bundle {
    val coreClk = in Bool
    val coreReset = in Bool
  val coreClockDomain = ClockDomain(
    clock = io.coreClk,
    reset = io.coreReset,
    config = ClockDomainConfig(
      clockEdge
                      = RISING,
      resetKind
                       = ASYNC,
      resetActiveLevel = HIGH
                                                             myCoreClockedRegister
  val coreArea = new ClockingArea(coreClockDomain) {
    val myCoreClockedRegister = Reg(UInt(4 bit))
    //...
```

Memory

```
//Memory of 1024 Bool
val syncRam = Mem(Bool, 1024)
val asyncRam = Mem(Bool, 1024)

//Write them
syncRam(5) := True
asyncRam(5) := True

//Read them
val syncRam = mem.readSync(6)
val asyncRam = mem.readAsync(4)
```

Function

```
// Input RGB color
val r,g,b = UInt(8 bits)
// Define a function to multiply a UInt by a scala Float value.
def coefMul(value : UInt,by : Float) : UInt = (value * U((255*by).toInt,8 bits) >> 8)
//Calculate the gray level
val\ gray = coefMul(r, 0.3f) +
           coefMul(g, 0.4f) +
           coefMul(b, 0.3f)
```

Function, User utils (1)

```
case class Color(channelWidth: Int) extends Bundle {
  val r,g,b = UInt(channelWidth bits)
  def +(that: Color): Color = {
    val result = Color(channelWidth)
    result.r := this.r + that.r
    result.g := this.g + that.g
    result.b := this.b + that.b
    return result
```


Function, User utils (2)


```
class ColorSumming(sourceCount : Int, channelWidth : Int) extends Component {
    val io = new Bundle {
        val sources = in Vec(Color(channelWidth), sourceCount)
        val result = out(Color(channelWidth))
    }


    var sum = io.sources(0)
    for (i <- 1 until sourceCount) {
        sum \= sum + io.sources(i)
    }
    io.result := sum
}</pre>
```

Advanced examples



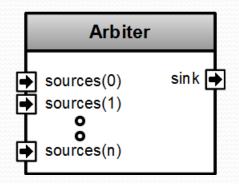

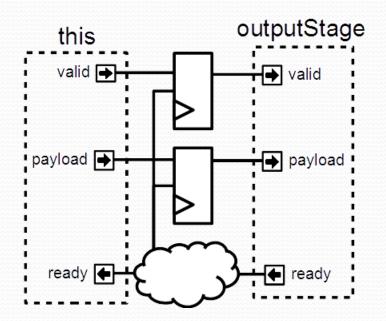

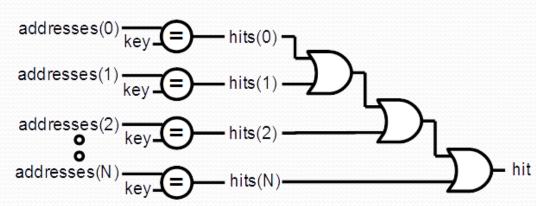

Functional programming

```
val addresses = Vec(UInt(8 bits),4)
val key = UInt(8 bits)
val hits = addresses.map(address => address === key)
val hit = hits.reduce((a,b) => a | | b)
addresses(2)
addresses(N)
```

Basic abstractions

```
val timeout = Timeout(1000)
when(timeout){  //implicit conversion to Bool
  timeout.clear() //Clear the flag and the internal counter
//Create a counter of 10 states (0 to 9)
val counter = Counter(10)
              //When called it reset the counter. It's not a flag
counter.clear()
counter.increment() //When called it increment the counter. It's not a flag
counter.value //current value
counter.valueNext //Next value
counter.willOverflow //Flag that indicate if the counter overflow this cycle
when(counter === 5){ ...}
```

Flow, Stream

Stream components

```
class Fifo[T <: Data](payloadType: T, depth: Int) extends Component {</pre>
  val io = new Bundle {
    val push = slave Stream (payloadType)
                                                                             Fifo
    val pop = master Stream (payloadType)
                                                                       push
                                                                                    pop
  //...
class Arbiter[T <: Data](payloadType: T, portCount: Int) extends Component {</pre>
  val io = new Bundle {
    val sources = Vec(slave(Stream(payloadType)), portCount)
                                                                           Arbiter
    val sink
                 = master(Stream(payloadType))
                                                                                    sink 🗐
                                                                       sources(0)
                                                                       sources(1)
                                                                       sources(n)
```

Stream functions


myStreamA <-< myStreamB

```
case class Stream[T <: Data](payloadType: T) extends Bundle {</pre>
 // ...
  def connectFrom(that: Stream[T]) = {
                                                                               outputStage
                                                            this
    // some connections between this and that
                                                            valid →
  def stage(): Stream[T] = {
    val outputStage = Stream(dataType)
    val validReg
                     = RegInit(False)
                                                          payload 🗪
                                                                                  payload
    val payloadReg = Reg(payloadType)
    // some logic
    return outputStage
                                                            ready 🗲
  def << (that: Stream[T]) = this.connectFrom(that)</pre>
  def <-< (that: Stream[T]) = this << that.stage()</pre>
val myStreamA,myStreamB = Stream(UInt(8 bits))
```


Scala is here to help you

```
class SinusGenerator(resolutionWidth: Int,sampleCount: Int) extends Component {
  val io = new Bundle {
    val sin = out SInt (resolutionWidth bits)
  def sinTable = (0 until sampleCount).map(sampleIndex => {
    val sinValue = Math.sin(2 * Math.PI * sampleIndex / sampleCount)
    S((sinValue * ((1 << resolutionWidth) / 2 - 1)).toInt, resolutionWidth bits)
  })
            = Mem(SInt(resolutionWidth bits), initialContent = sinTable)
  val phase = CounterFreeRun(sampleCount)
  io.sin := rom.readSync(phase)
```

Design introspection

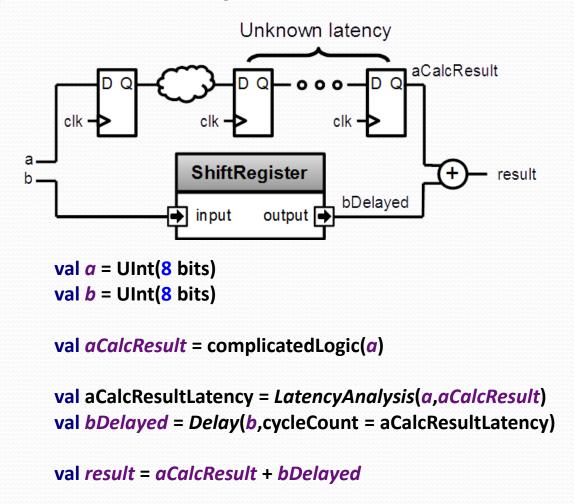

Meta-hardware description examples

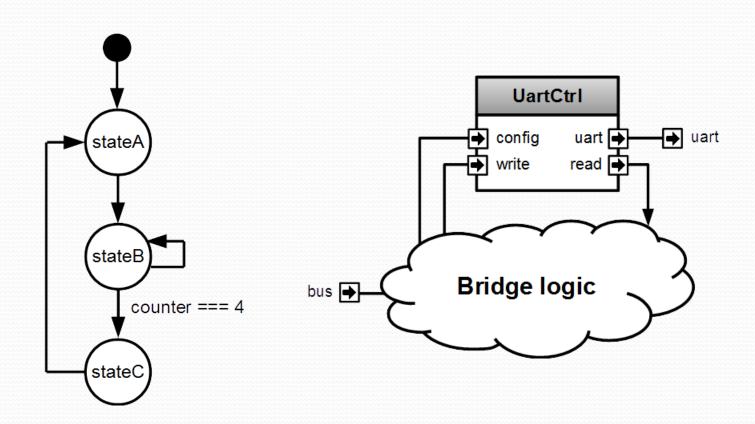


FSM

- They could be defined with regular syntax (Enum, Switch)
- You can also use a much more friendly syntax, fully integrated, with following features:
 - onEntry / onExit / whenIsActive / whenIsNext blocs
 - State with inner FSM
 - State with multiple inner FSM (parallel execution)
 - Delay state
 - You can extends the syntax by defining new state types

FSM style A

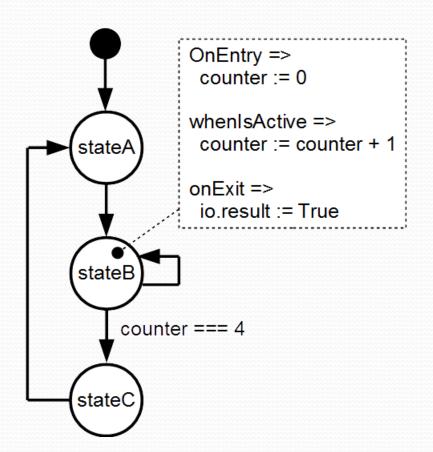
```
val io = new Bundle{
  val result = out Bool
}
```



```
val fsm = new StateMachine{
  io.result := False
  val counter = Reg(UInt(8 bits)) init (0)
  val stateA : State = new State with EntryPoint{
    whenIsActive (goto(stateB))
  val stateB : State = new State{
    onEntry(counter := 0)
    whenIsActive {
      counter := counter + 1
      when(counter === 4){
        goto(stateC)
    onExit(io.result := True)
  val stateC : State = new State{
    whenIsActive (goto(stateA))
```

FSM style B

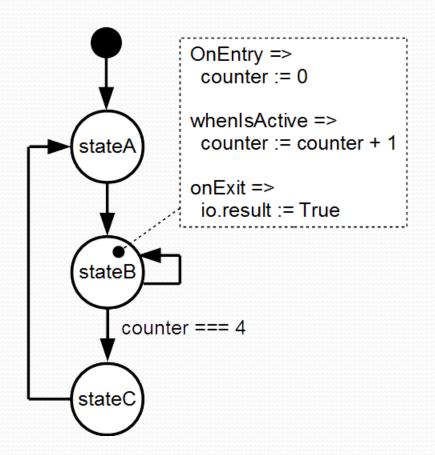
```
val io = new Bundle{
  val result = out Bool
}
```




```
val fsm = new StateMachine{
  val stateA = new State with EntryPoint
  val stateB = new State
  val stateC = new State
  val counter = Reg(UInt(8 bits)) init (0)
  io.result := False
  stateA
    .whenIsActive (goto(stateB))
  stateB
    .onEntry(counter := 0)
    .whenIsActive {
      counter := counter + 1
      when(counter === 4){
        goto(stateC)
    .onExit(io.result := True)
  stateC
    .whenIsActive (goto(stateA))
```

Bus Slave Factory

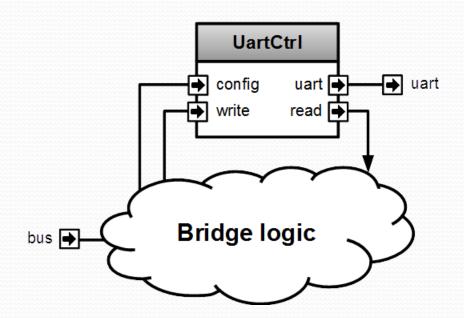 Imagine you want to control an UART controller from a bus (for example AMBA-APB), you will have to implement a "bridge logic".




Let's detail the situation

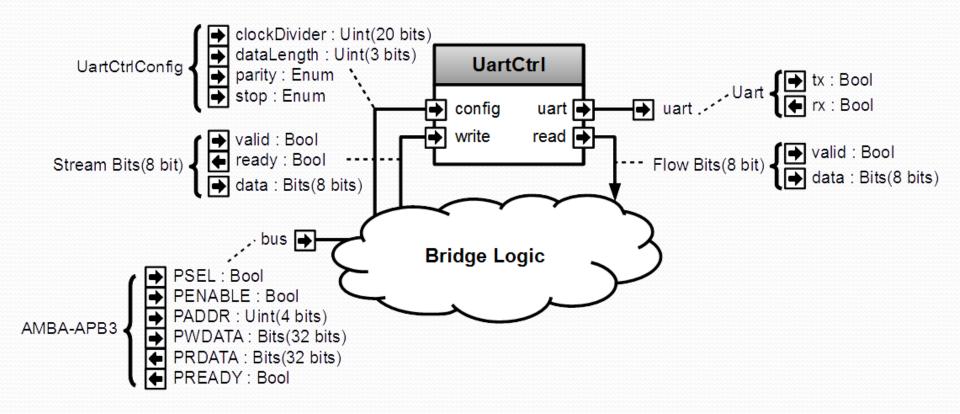

IO / instances / direct connections

```
class Apb3UartCtrl(rxFifoDepth : Int) extends Component {
 val io = new Bundle {
  val bus = slave(Apb3(addressWidth = 4, dataWidth = 32))
  val uart = master(Uart())
// Instantiate an simple UART controller
 val uartCtrl = new UartCtrl()
//Connect its UART bus
 io.uart <> uartCtrl.io.uart
//Here we have to implement the "bridge logic".
//All the code of next slides should be inserted there
//...
```

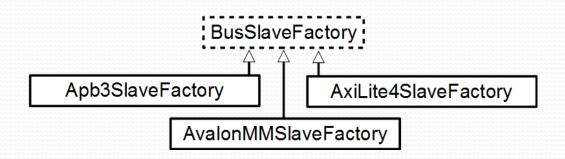 Apb3SlaveFactory is able to create some "bridge logic" by using an abstract way. Let's use it!




val busCtrl = Apb3SlaveFactory(io.bus)

Make the clockDivider readable/writable by the bus

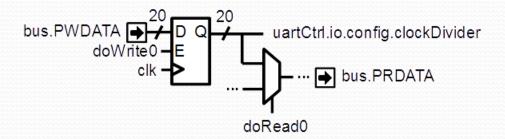
```
// Ask the busCtrl to create a readable/writable register at the address 0 // and drive uartCtrl.io.config.clockDivider with this register busCtrl.driveAndRead(uartCtrl.io.config.clockDivider,address = 0)
```





Make the frame config readable/writable by the bus

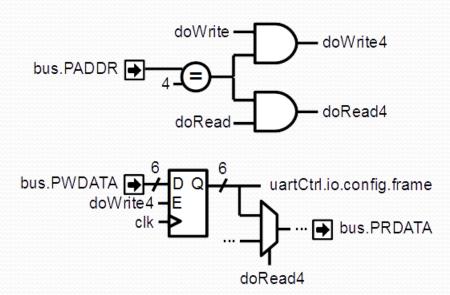// Do the same thing than previously but for uartCtrl.io.config.frame at the address 4 busCtrl.driveAndRead(uartCtrl.io.config.frame,address = 4)




Allow the bus to emit UART write requests

```
// Ask the busCtrl to create a writable Flow[Bits] (valid/payload) at the address 8.

// Then convert it into a stream, add a register register stage and connect it to the uartCtrl.io.write


val writeFlow = busCtrl.createAndDriveFlow(Bits(8 bits),address = 8)

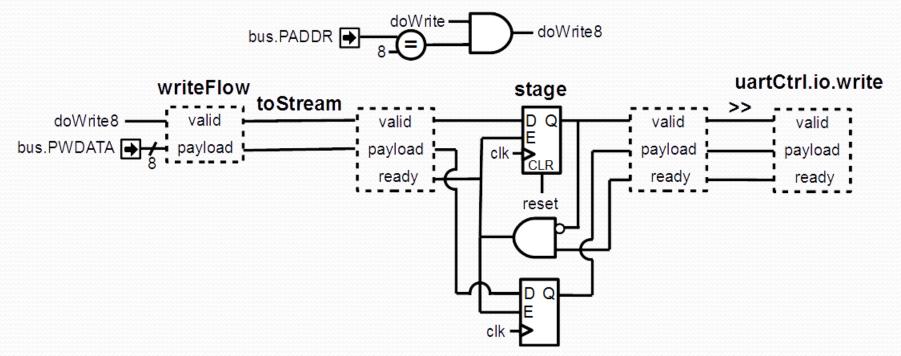
writeFlow.toStream.stage >> uartCtrl.io.write
```



Allow the bus to get the occupancy of the write buffer

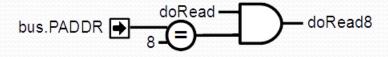// To avoid losing writes commands between the Flow to Stream transformation just above, // make the occupancy of the uartCtrl.io.write readable at address 8 busCtrl.read(uartCtrl.io.write.valid,address = 8)



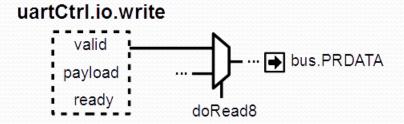

Allow the bus to read received UART frames through a FIFO

```
// Take uartCtrl.io.read, convert it into a Stream, then connect it to the input of a FIFO

// Then make the output of the FIFO readable at the address 12 by using a non blocking protocol

// (bit 31 => data valid, bits 7 downto 0 => data)


val readStream = uartCtrl.io.read.toStream.queue(rxFifoDepth)

busCtrl.readStreamNonBlocking(readStream,address = 12,validBitOffset = 31,payloadBitOffset = 0)

bus.PADDR doRead doRead queue(rxFifoDepth)

queue(rxFifoDepth)

partCtrl io read
```

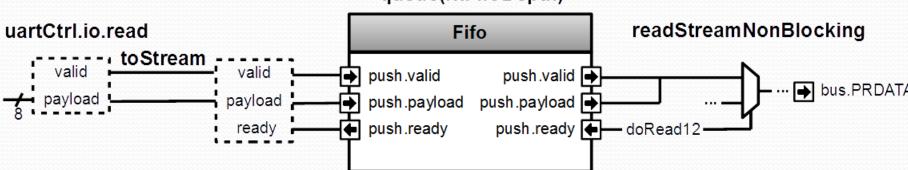

About FSM and Apb3SlaveFactory

Both aren't part of Spinal core but are implemented on the top of it in the Spinal lib. Which mean these tools were created without any special interaction or special knowledge of the Spinal compiler.

They are only a mix of Scala OOP/FP with some Spinal basic syntax to generate the right hardware!

About Scala

- Free Scala IDE (eclipse, intelij)
 - Highlight syntax error
 - Renaming flexibility
 - Intelligent auto completion
 - Code's structure overview
 - Navigation tools
- Allow you to extend the language
- Provide many libraries

Spinal work perfectly on FPGA


- RISCV CPU, 5 stages, 1.15 DMIPS/Mhz
 - MUL/DIV
 - Instruction/Data cache
 - Interrupts
 - JTAG debugging
- Avalon/APB UART
- Avalon VGA
- Pipelined and multi-core fractal accelerator


About Spinal project

- Completely open source :
 - https://github.com/SpinalHDL/SpinalHDL
- Online documentation :
 - https://spinalhdl.github.io/SpinalDoc/
- Ready to use base project :
 - https://github.com/SpinalHDL/SpinalBaseProject
- Communication channels :
 - spinalhdl@gmail.com
 - https://gitter.im/SpinalHDL/SpinalHDL
 - https://github.com/SpinalHDL/SpinalHDL/issues

End / reserve slides

Meta-hardware description

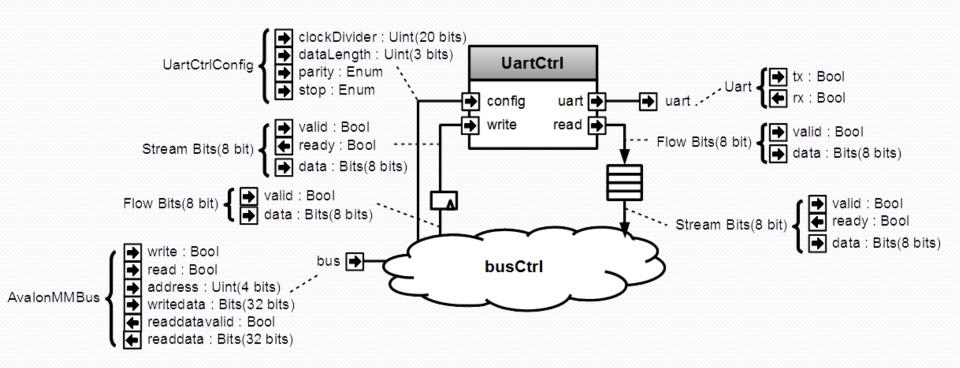

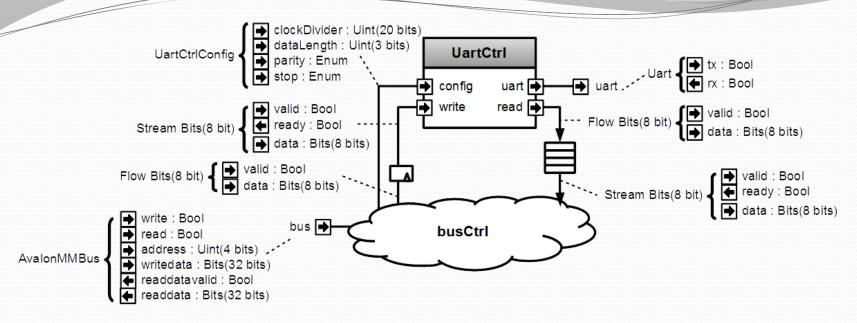

Name	Туре	Access	Address	Description
clockDivider	UInt	RW	0	Set the UartCtrl clock divider
frame	UartCtrlFrameConfig	RW	4	Set the dataLength, the parity and the stop bit configuration
writeCmd	Bits	w	8	Send a write command to the UartCtrl
writeBusy	Bool	R	8	Bit 0 => zero when a new writeCmd could be sent
read	Bool / Bits	R	12	Bit 7 downto 0 => fifo pop payload Bit 31 => fifo pop valid

```
class AvalonUartCtrl(uartCtrlConfig : UartCtrlGenerics, rxFifoDepth : Int) extends Component{
  val io = new Bundle{
    val bus = slave(AvalonMM(...))
    val uart = master(Uart())
  val uartCtrl = new UartCtrl(uartCtrlConfig)
  io.uart <> uartCtrl.io.uart
  val busCtrl = AvalonMMSlaveFactory(io.bus)
  //Make clockDivider register
  busCtrl.driveAndRead(uartCtrl.io.config.clockDivider, address = 0)
 //Make frame register
  busCtrl.driveAndRead(uartCtrl.io.config.frame, address = 4)
 //Make writeCmd register
  val writeFlow = busCtrl.createAndDriveFlow(Bits(uartCtrlConfig.dataWidthMax bits), address = 8)
  writeFlow.toStream.stage() >> uartCtrl.io.write
  //Make writeBusy register
  busCtrl.read(uartCtrl.io.write.valid, address = 8)
  //Make read register
  busCtrl.readStreamNonBlocking(uartCtrl.io.read.toStream.queue(rxFifoDepth),
                                  address = 12, validBitOffset = 31, payloadBitOffset = 0)
                                                                                                  52
```